TD1: Introduction to Logisim, counter by 4 and ALU

September 29th, 2021

INFO0012 - Computation Structures

For this course, you will have to build a simple – but working – computer called the β -machine in the Logisim simulation environment. This first practical session will introduce you to the Logisim software. You will build and simulate your first circuits: a counter by 4 and a ALU (arithmetic–logic unit). These components will then be useful for your future β -machine.

- First, install the original version of Logisim from eCampus (Software / Logisim). You might need
 to install Java in order for the software to run. Familiarize yourself with the software. You can
 find the documentation on the website. You may also want to watch the short tutorial podcast
 available on eCampus (Theoretical sessions / 99 Logisim).
- 2. In Logisim, build a binary counter with the following properties:
 - The counter must hold a 32-bit value and count by steps of 4 at every clock cycle. You can use every building block available in Logisim you might need
 - Your circuit must include a single bit input signal to reset the counter, setting back its value to 0 when enabled, and a 32-bit output reflecting the current value of the counter
 - The counter must count up to the last 4 digits of your student number (e.g. up to 8765 for student ID 20198765), then come back to 0. If your student number is not a multiple of 4, you can round at the next multiple of 4 (8768 in our example).

Simulate your circuit to check its proper functioning.

- 3. Build an ALU with the following properties:
 - It should have two 32-bit inputs A and B, a 32-bit output and a 4-bit input ALUFN to select the operation.
 - It should support the same operations as the ALU presented in the theoretical course.
 - You may use plexers, adders, shifters, comparator, and all other logic and arithmetic boxes available in Logisim with any bit width. It would basically look like on slide 4-27. On slide 4-27, only the comparison box is not a Logisim library object (but it is made of a very few Logisim library objects).

Simulate your circuit and make sure that every operation works properly and gives correct answers, e.g. with A=6 and B=3.

Good luck and have fun building your first computer from scratch!

"If you wish to make an apple pie from scratch, you must first invent the universe."

- Carl Sagan, Cosmos